

VLSI LABORATORY [EC39004]

LAB REPORT - 8


Kundrapu N R Sai Akash [20EC10043]
Nagiseti Rithihas [20EC10049]

OBJECTIVE:


- 1) Implement 2 bit adder using pass transistors*
- 2) Implement 4:1 mux using transmission gates*

CIRCUIT DIAGRAMS:

● 2 Bit Adder (Pass Transistors)

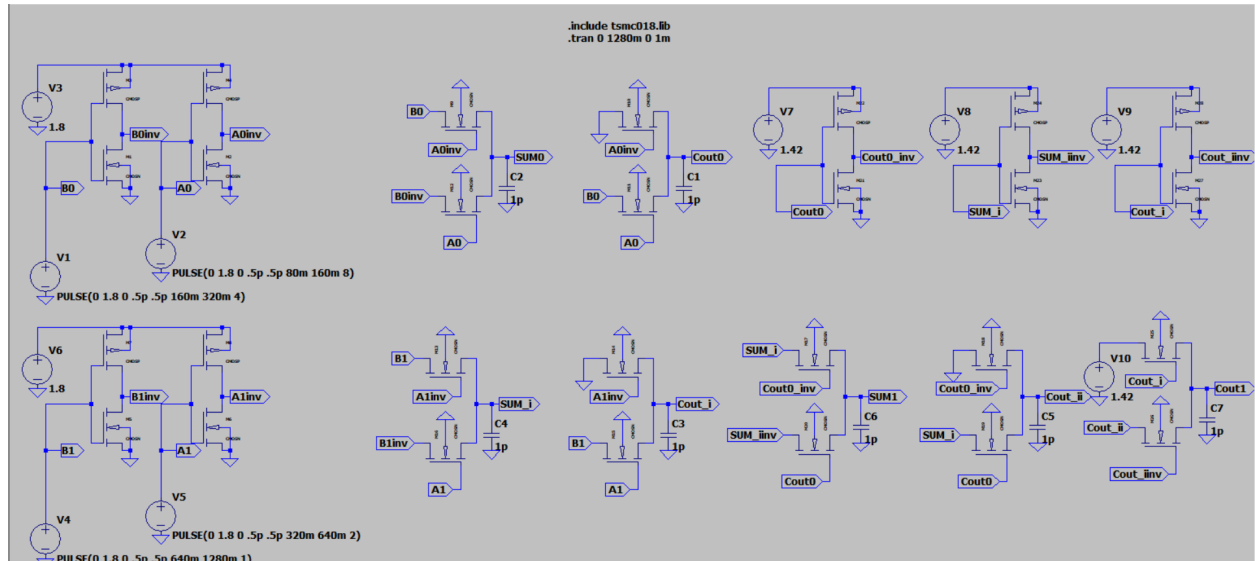


● 4:1 MUX (Transmission Gates)

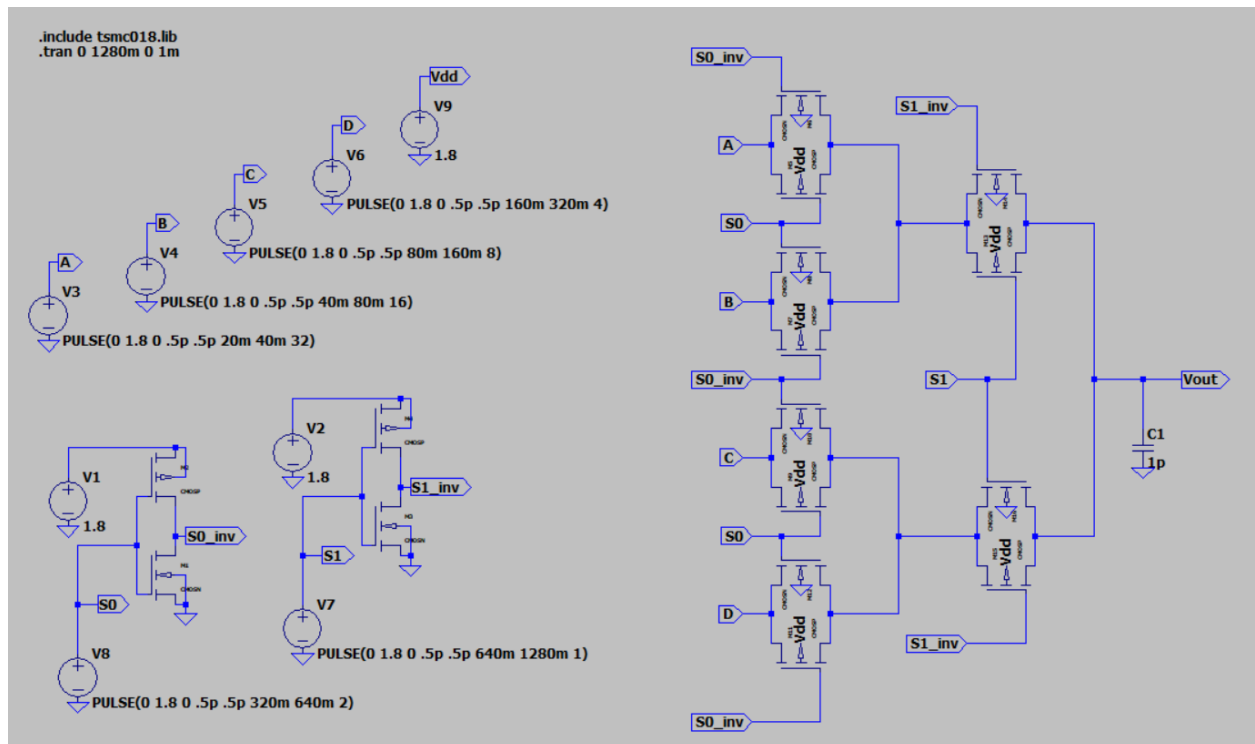


OUTPUT WAVEFORMS:

- *2 Bit Adder (Pass Transistors)*

 

- *4:1 MUX (Transmission Gates)*

 

DISCUSSION:

1. 2 Bit Adder (Pass Transistors)

- In order to implement a 2bit full adder, we will make use of a 1bit half adder circuit which consists of an AND to give carry output and XOR gate to give sum output.
- We will need 2half adders and an OR gate to realize a 1bit full adder.
- So, in total, we need 3half adders and an OR gate to realize 2bit full adder.
- In order to realize the AND, XOR, OR gates, we are going to use pass transistor logic(PTL).
- Pass Transistor Logic (PTL) are generally superior to CMOS circuits interms of delay and power consumption.
- As we observe in the output waveform plots, the values of Sum0, Sum1, Cout1 are accurate to the expected values.

$$\text{Sum0} = A0 \wedge B0$$

$$\text{Sum1} = A1 \wedge B1 \wedge \text{Cout0}$$

$$\text{Cout1} = A1 \cdot B1 + \text{Cout0} \cdot (A1 \wedge B1)$$

- We observe that, there is still a bit of loss at each PTL gate level transmission.
- Initially our input was at $V_{dd}=1.8V$. After the first stage of half adder, we see a fall in V_{max} which is now close to 1.42V, we can see in the plot for Sum0.
- For Sum1 and Cout1, the maximum voltage value goes further down to around 1.1V.
- In order to obtain inverted voltages for some of the pins, we are still using static CMOS logic, where the V_{dd} level is set according to the input's max voltage.
- We see small fluctuations in Sum1 and Cout1, which is most probably caused because of the different levels of max voltage for input pins(1.8V) and 1st stage pins(1.42V).

2. 4:1 MUX (Transmission Gates)

- We realize 4:1 MUX using 3' 2:1 MUX, where we have 4input bits and 2 select bits.
- Our 4:1 MUX will send one of the 4 input bits as output bit according a specific select bit combination.
- In our circuit, if select line is 00, $V_{out} = A$, if 01, $V_{out} = B$, if 10 $V_{out} = C$, if 11 $V_{out} = D$.
- We can write this in the form of a boolean logic,
$$V_{out} = A \cdot S0' \cdot S1' + B \cdot S0 \cdot S1' + C \cdot S0' \cdot S1 + D \cdot S0 \cdot S1$$
- As we can observe the output waveform, we can clearly see the multiplexer working correctly.
- We implemented this circuit using transmission gates which are generally used in these analog multiplexers and bilateral switches.
- The advantage of this logic is that it can be implemented using less transistors compared to traditional CMOS logic, but this logic consumes more power.